

Lab 3 Submission

Ethan Vosburg
Cal Poly SLO
Fall 2023
CPE 133
Instructor: Gary Perks
October 18, 2023

1 Introduction

The goal of this lab was to design and program a logic circuit that adds two 4bit numbers and then displays them on the seven segment display. This lab was a success and I was able to complete all of the tasks.

2 Video of Working Project

Linked here is a video of the working project: [Project Video](#)

3 Simulation

 


Figure 1: Vivado Simulation

4 Elaborated Design

Presented below is the elaborated design of the project generated by Vivado.

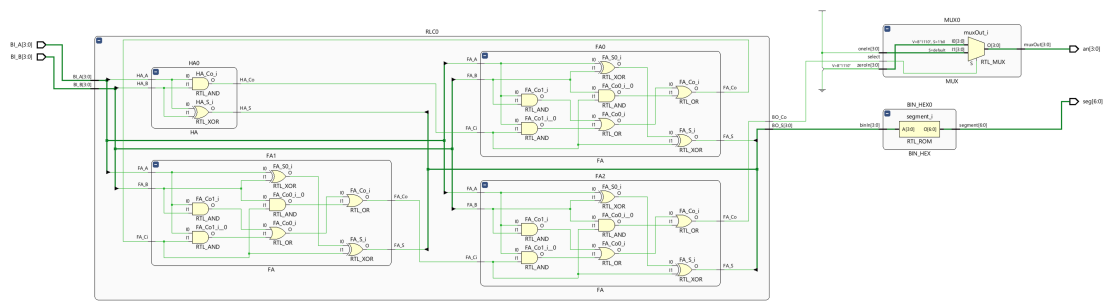


Figure 2: Elaborated Design

5 Error Log

There were no errors or significant warnings in the Vivado log as shown below.

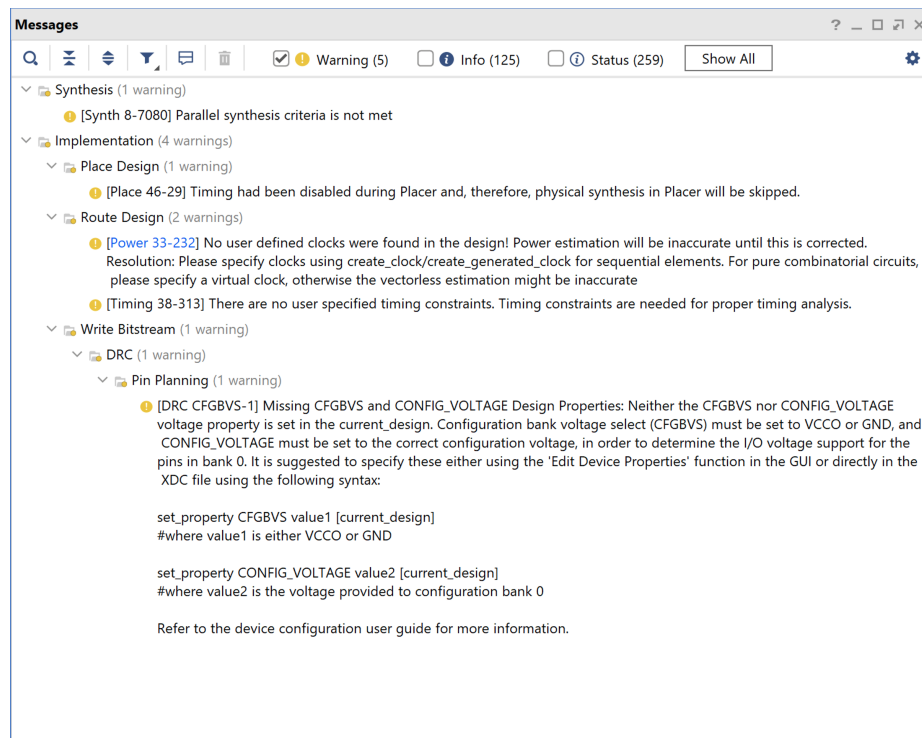


Figure 3: Error and Warning Log